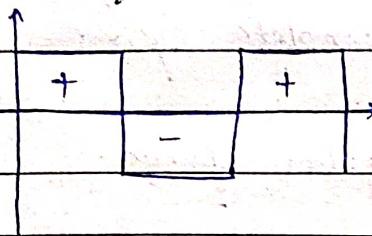



Module - 2 AC Fundamentals

"AC Quantity" The Quantity like (V, I) whose magnitude are directional change w.r.t time. (Polarity)


Square Wave




Triangular Wave

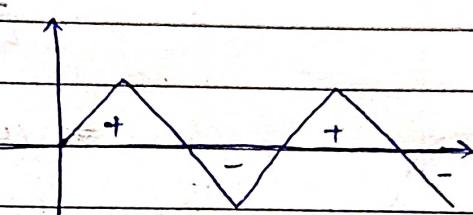

Trapezoidal waves

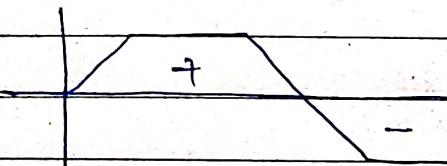


Sin waves

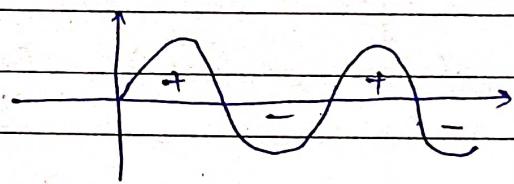


"DC Quantity" whose magnitude may or may not change, DC Quantity is defined with one which may change its magnitude but does not change the dirⁿ


Pure D.C.

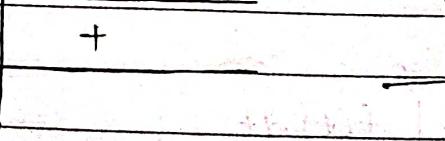

Pulsating D.C.


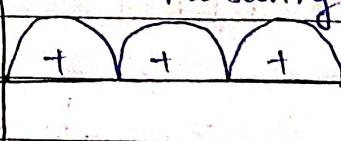


H.W. Rectifi.

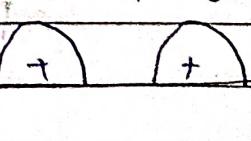

* The Shape of Curve of V, I when plotted against time as abscissa called waveform.

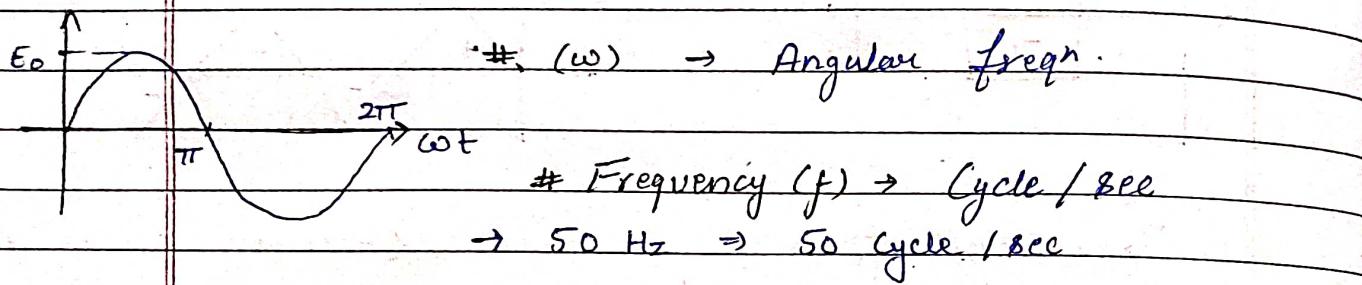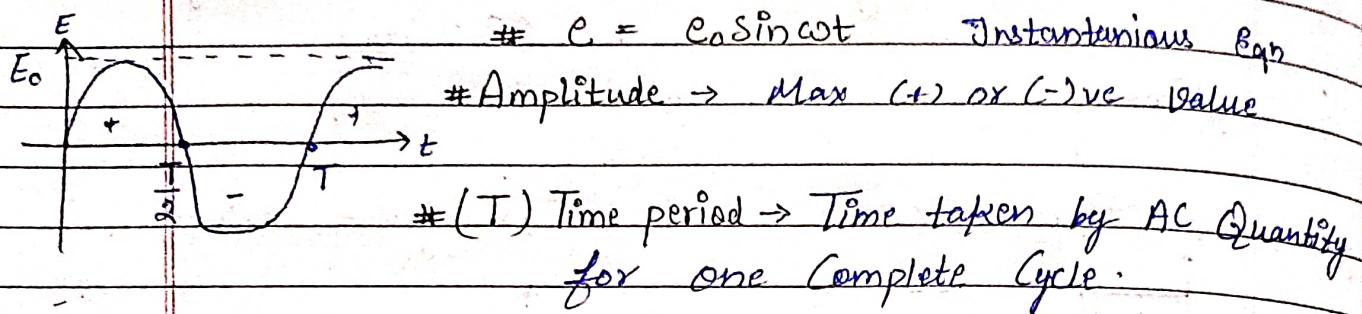→ alternating voltage and Current means sinusoidal voltage and current otherwise started



$$T = \frac{1}{f}$$

Average value \rightarrow Average value of A.C. is equal to value of Direct Current which transfers across any circuit the same charge as it transferred by A.C.


→ Let $f(t)$ is a periodic fxn with fundamental period $= (T)$

$$f_{avg} = \frac{1}{T} \cdot \int_0^T f(t) dt$$

Waveforms \rightarrow

a) Symmetrical Waveforms \rightarrow

$$F_{avg} = 0$$

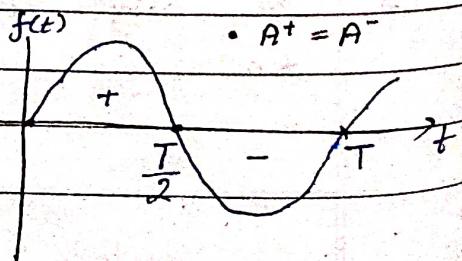

◻ Symm \rightarrow avg, rms \rightarrow half Cycle
 Unsym \rightarrow " " \rightarrow full "

Page No.:

Date: / /

(3)


\rightarrow we always Consider "Half Cycle" for Calculating Avg in "Symmetrical" Waveform.

b) (i) Unsymmetrical Waveform \rightarrow


$$F_{avg} = \frac{1}{2\pi} \int_0^{2\pi} f(\theta) d\theta$$

'OR'
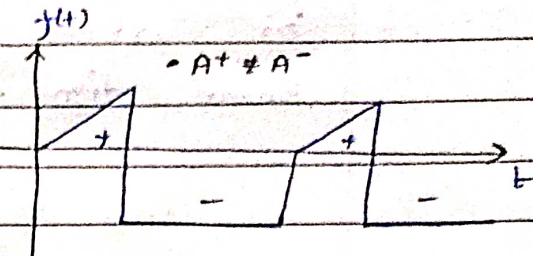
$$F_{avg} = \frac{1}{T} \int_0^T f(t) dt$$



Sinusoidal Quantity

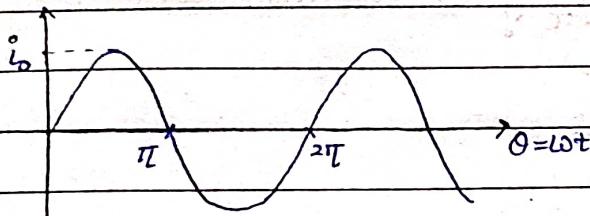

$$i = i_0 \sin(\omega t)$$

$$i_{avg} = \frac{1}{2\pi} \int_0^{2\pi} i d\theta$$

$$i_{avg} = -\frac{i_0}{2\pi} [\cos(\omega t)]_0^{2\pi}$$

$$= -\frac{i_0}{2\pi} [1 - 1]$$

$$\boxed{i_{avg} = 0}$$

\Rightarrow for Half Cycle \rightarrow

$$i_{avg} = -\frac{1}{\pi} \int_0^\pi i d\omega t$$


$$i_{avg} = \frac{2i_0}{\pi} = 0.636 i_0$$

\rightarrow R.M.S. value (root mean square value) \rightarrow
 (Heat Dependent)

(Effective Value)

let $f(t)$ is a periodic fxn with Time period = T
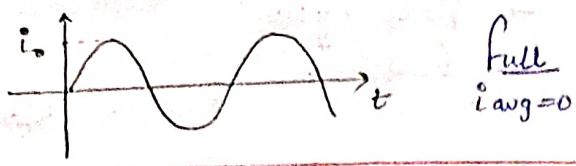
$$F_{rms} = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt}$$



full
 $i_{avg} = 0$

Half
 $i_{avg} = \frac{2i_0}{\pi}$

Page No.:
Date: / /


RMS - The rms value is that value of current which produces same amount of heat for a given time as when alternating voltage when or current applied to some circuit for same time.

$$i_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T (i_0 \sin \omega t)^2 dt}$$

$$= \sqrt{\frac{i_0^2}{2\pi} \int_0^T (1 - \cos 2\omega t) dt}$$

$i_{rms} = \frac{i_0}{\sqrt{2}}$

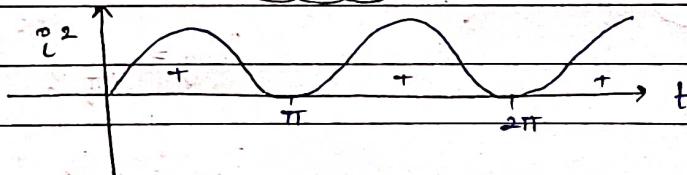

Form factor (K_f) = $\frac{\text{rms value}}{\text{average value}}$


Peak factor (K_p) = $\frac{\text{Peak value}}{\text{rms value}}$

Sinusoidal \rightarrow

$$K_f = \frac{e_0 / \sqrt{2}}{\alpha e_0 / \pi} = \frac{\pi}{2\sqrt{2}} = 1.11$$

$$K_p = \frac{e_0}{e_0 / \sqrt{2}} = \sqrt{2} = 1.414$$

Full wave rectifier Output \rightarrow

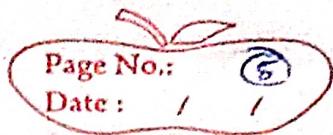

$$\bar{V}_{avg} = \frac{1}{\pi} \int_0^{\pi} V dt$$

$$V = |V_0 \sin \omega t|$$

$$\bar{V}_{avg} = \frac{2 V_0}{\pi}$$


$$8 \quad V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} V^2 dt}$$

$$= \sqrt{\frac{1}{\pi} \left(\frac{V_0^2}{2}\right) \int_0^{\pi} (1 - \cos 2\omega t) dt}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

Half Wave rectifier Output
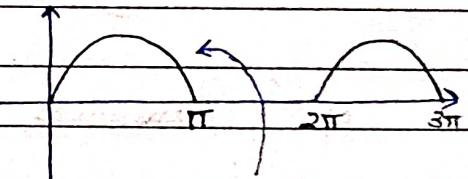
$$\bar{i}_{avg} = \frac{1}{2\pi} \int_0^{\pi} i dt + \int_{\pi}^{2\pi} 0 \cdot dt$$



$$\bar{i}_{avg} = \frac{i_0}{\pi}$$

$$i = i_0 \sin \omega t$$

$$8 \quad i_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2 dt}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{\pi} (i_0 \sin \omega t)^2 dt + \int_{\pi}^{2\pi} 0^2 dt}$$

$$= \sqrt{\frac{i_0^2}{4\pi} \left[\omega t - \frac{\sin \omega t}{\omega} \right]_0^{\pi}}$$


$$= \sqrt{\frac{i_0^2}{4\pi} \times \pi}$$

$$i_{rms} = \frac{i_0}{2}$$

$$K_p = \frac{i_0}{i_0/2} = 2$$

$$K_f = \frac{i_0/2}{i_0/\pi} = \frac{\pi}{2} = 1.57$$

'Square Wave'

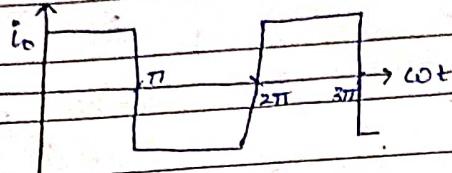

$$\Rightarrow i_{avg} = \frac{1}{\pi} \int_0^{\pi} i_o d\omega t$$

$$= \frac{1}{\pi} \int_0^{\pi} i_o \sin \omega t d\omega t$$

$$\# P_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} i^2 d\omega t}$$

$$= \sqrt{\frac{i_o^2}{\pi} \left[\omega t \right]_0^{\pi}}$$

$$= i_o$$


$$= \frac{i_o}{\pi} \left[\omega t \right]_0^{\pi}$$

$$= i_o$$


$$\# f_g = 1$$

$$K_p = 1$$

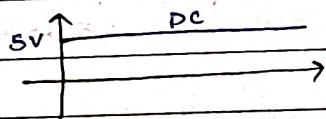(c) Constant Waveform \rightarrow $avg = rms$ value




$$avg = 5 = rms$$

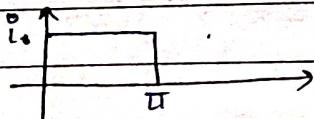

$$avg = \frac{\text{area}}{\text{length}} = \frac{\pi i_o}{\pi} = i_o$$

(d) Triangular Waveform \rightarrow

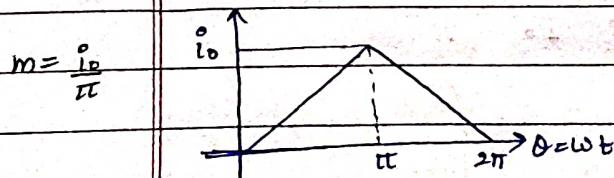


\Rightarrow Let us assume it is symmetrical waveform \rightarrow

\Rightarrow half Cycle (2π)

\Rightarrow Quarter Cycle (π)
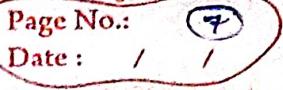
$$i_{avg} = \frac{1}{\pi} \int_0^{\pi} i_o d\omega t$$



$$= \frac{1}{\pi} \int_0^{\pi} \frac{i_0}{\pi} \sin \theta d\theta$$

$$= \frac{1}{\pi^2} i_0 \left[\theta \right]_0^{\pi}$$

$$i_{avg} = \frac{i_0}{2}$$

$$\& i_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} i^2 d\theta} = \sqrt{\frac{1}{\pi} \times \frac{i_0^2}{\pi^2} \int_0^{\pi} \sin^2 \theta d\theta}$$

$$i_{rms} = \frac{i_0}{\sqrt{3}}$$


$$K_f = \frac{i_0/\sqrt{3}}{i_0/2} = \frac{2}{\sqrt{3}} = 1.15$$

$$K_p = \frac{i_0}{i_0/\sqrt{3}} = \sqrt{3} = 1.732$$

\therefore Area = $i_0 \pi$, length = 2π

$$avg = \frac{i_0 \pi}{2\pi} = \frac{i_0}{2}$$

Ques:

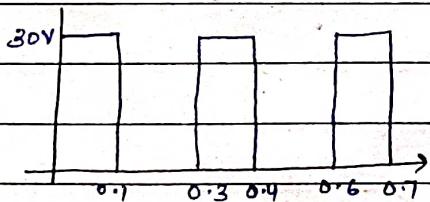

$$\# V_{avg} = \frac{1}{0.3} \int_0^{0.3} f(t) dt$$

$$= \frac{30 \times 0.1}{0.3}$$

$$= 10$$

$$\# V_{rms} = \sqrt{\frac{1}{0.3} \int_0^{0.1} (30)^2 dt}$$

$$= \sqrt{\frac{30 \times 30 \times 0.1}{0.3}}$$

$$= \sqrt{300} = 10\sqrt{3} = 17.32$$

$$K_f = \frac{10\sqrt{3}}{10} = 1.732$$

$$K_p = \frac{30}{10\sqrt{3}} = \sqrt{3}$$

Waveform	rms	avg	Kf	Rp
Sin wave	$i_0/\sqrt{2}$	$2i_0/\pi$	1.11	1.41
Full wave rec.	$i_0/\sqrt{2}$	$2i_0/\pi$	1.11	1.41
Half wave rec.	$i_0/2$	i_0/π	1.57	2
Square wave	i_0	i_0	1	1
Triangular	$i_0/\sqrt{3}$	$i_0/\sqrt{2}$	$2/\sqrt{3}$	$\sqrt{3}$

Ques # A sinusoidally varying alternating current of frequency 60 Hz with Max value of 15 amp.

- What is instantaneous Eqn
- Find value of Sinusoidal after $\frac{1}{200}$ sec
- Find time taken to reach Current $i = 10$ amp.
- Find the average.

$$i = 15 \sin 120\pi t$$

$$ii) i = 15 \sin 120\pi \times \frac{1}{200} = 15 \sin \frac{3\pi}{5} = 14.27$$

$$iii) i = 15 \sin 120\pi t$$

$$10 = 15 \sin (120\pi t)$$

$$t = \frac{1}{120\pi} \sin^{-1}(10/15)$$

$$iv) avg = \frac{2i_0}{\pi} = \frac{2 \times 15}{3.14} = 9.54$$

Ques # An AC Current has rms value of 40 amp and 50Hz freq. write instantaneous Eqn and find its value 2×10^{-3} sec after passing through max C.G value

$$I_{rms} = 40 A$$

$$= i_0/\sqrt{2} \Rightarrow i_0 = 40\sqrt{2}$$

$$\therefore i = 40\sqrt{2} \sin(100\pi t)$$

$$f = 50 \text{ Hz} \Rightarrow T = \frac{1}{f} = 0.02 \text{ sec}$$



\Rightarrow Time to Complete Half Cycle = 10 msec
 " " have Max value = 5 msec

$$\Rightarrow t = 5 \times 10^{-3} + 2 \times 10^{-3} = 7 \times 10^{-3}$$

$$\text{So } i = 40\sqrt{2} \sin(100\pi \times 7 \times 10^{-3}) \\ = 45.76 \text{ Amp.}$$

→ Phasor Representation of AC Quantity

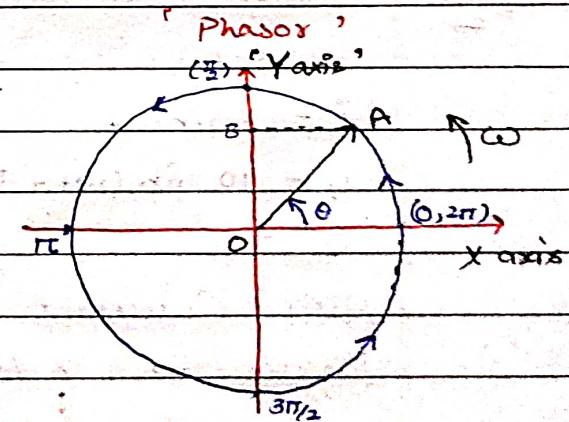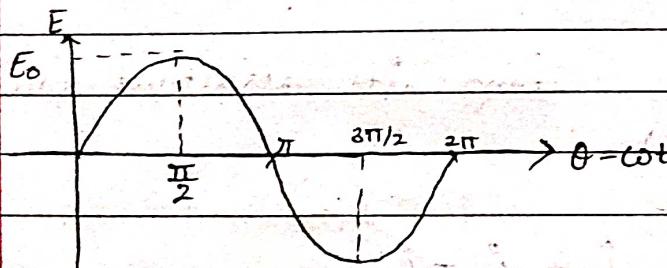For the soln of AC problems it is good to represent a sinusoidal Quantity either V or I by the line of definite length rotating Counter Clockwise dirn with same angular velocity as that of sinusoidal Quantity Such a Rotating line is called phasor.



$$OB = OA \sin \theta$$


$$E = E_0 \sin(\omega t)$$

• Phasor is always drawn from phasor value.

Page No.:


Date: / /

I_1 lead I_2 by angle $\phi \rightarrow$

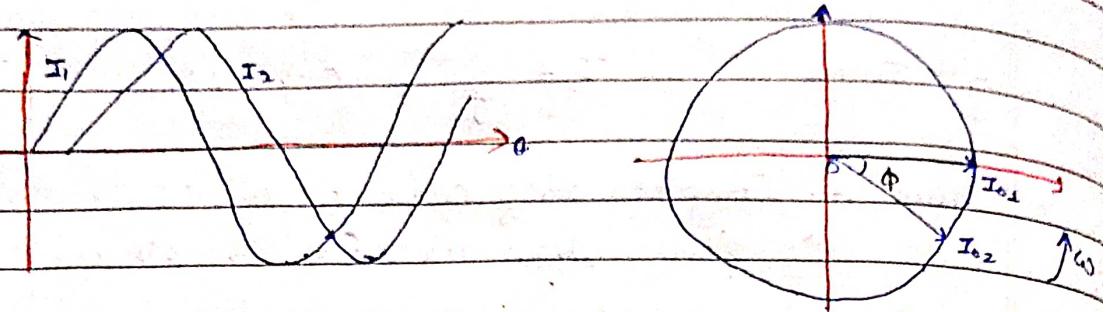

$\Rightarrow \phi \Rightarrow \text{Constant}$

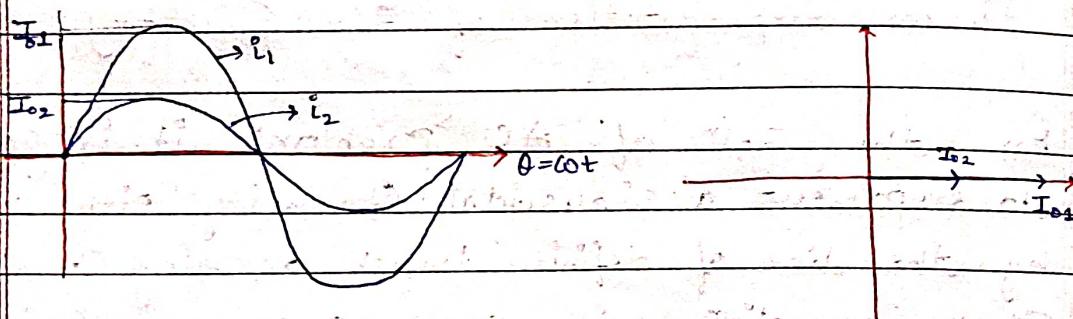I_1 and I_2 are in same phase \rightarrow



Graph

Ques: Two alternating Quantities

$$i_1 = 7 \sin \omega t$$

Find its resultant Current

$$i_2 = 10 \sin(\omega t + \pi/3)$$

$$\text{A.C. Current } i = i_1 + i_2$$

$$\text{Phasor} \rightarrow r \angle \theta \rightarrow (\text{Polar form}) = r(\cos \theta + j \sin \theta)$$

Magnit. Angle

$$= a + j(b) \rightarrow (\text{Rectangular form}) ; j = \sqrt{-1}$$

Real Imaginary

$$\overline{I}_1 = \text{Phase of } i_1$$

$$= \frac{7}{\sqrt{2}} 10^\circ = 4.94 10^\circ$$

$$= 4.94 (\cos 10^\circ + j \sin 10^\circ)$$

\bar{I}_2 = Phase of i_2

$$= \frac{10}{\sqrt{2}} \angle 60^\circ = 7.07 (\cos 60 + j \sin 60)$$

$$= (3.535) + j(6.1226)$$

$$\bar{I} = \bar{I}_1 + \bar{I}_2$$

$$= 4.94 + 3.535 + j(6.1226)$$

$$= 8.475 + j(6.1226) \rightarrow \text{Rect form}$$

$$= 10.455 \angle 35.84^\circ \rightarrow \text{Polar form}$$

$$\Rightarrow I_o = (10.455) \sqrt{2} \sin(\omega t + 35.84^\circ)$$

Ques: $V_1(t) = 30 \sin(314t + 45^\circ)$

$$V_2(t) = 60 \sin(314t + 60^\circ)$$

$$\bar{V}_1 = \frac{30}{\sqrt{2}} \angle 45^\circ = 14.99 + 14.99j$$

$$\approx 15 + 15j$$


$$\bar{V}_2 = \frac{60}{\sqrt{2}} \angle 60^\circ = 21.21 + j(36.736)$$

Ans $\bar{V} = \bar{V}_1 + \bar{V}_2 = 36.21 + j(51.736)$

$$= 63.14 \angle 55^\circ$$

$$V = V_0 \sin \omega t$$
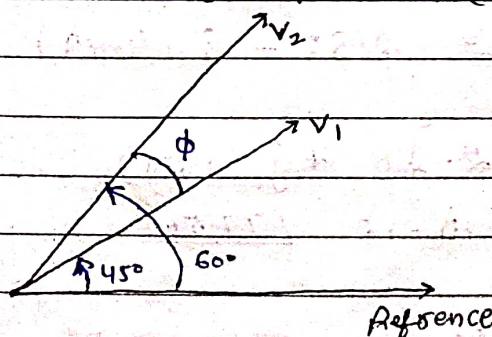
$$= 63.14 \sqrt{2} \sin(314t + 55^\circ)$$



$$\phi = 60^\circ - 45^\circ$$

$$= 15^\circ$$

Ques:

$$V_1 = 100 \sin 500t$$

$$V_2 = 200 \sin (500t + \pi/3)$$

$$V_3 = -50 \cos (500t) = 50 \sin (500t - \pi/2)$$

$$V_4 = 150 \sin (500t - \pi/4)$$

Find rms of Resultant

$$\bar{V}_1 = 70.7 \angle 0^\circ = 70.7$$

$$\bar{V}_2 = 141 \angle 60^\circ = 70.5 + j(122.10)$$

$$\bar{V}_3 = 35.35 \angle -90^\circ = -j(35.35)$$

$$\bar{V}_4 = 100.06 \angle -45^\circ = 75 - j(75)$$

$$\bar{V} = 216.12 + j(12.14)$$

$$= 216.750 \angle 3.2^\circ$$

$$\text{Resultant } V = 216.75 \sqrt{2} \sin (500t + 3.2^\circ)$$

Ques:

$$i_1 = 10 \sin (314t + \pi/4) \quad \text{find phase diff.}$$

$$i_2 = 8 \sin (314t - \pi/3) \quad \text{btw } i_1 \text{ & } i_2$$

Find difference of these Current.

$$\bar{I}_1 = \frac{10}{\sqrt{2}} \angle 45^\circ = 5 + j(5)$$

$$\bar{I}_2 = 8 \angle -60^\circ = 2.82 - j(4.89)$$

$$I = \bar{I}_1 - \bar{I}_2 = 2.18 + j(9.89)$$

$$= 10.12 \angle 77.56^\circ$$

Ans \Rightarrow

$$I = 10.12 \sqrt{2} \sin (314t + 77.62)$$

$$\Rightarrow \text{Phase diff. btwn } \bar{i}_1 \text{ & } \bar{i}_2 = \frac{\pi}{4} - \left(-\frac{\pi}{3}\right) = \frac{7\pi}{12}$$

$(\phi)_{\text{purely Resist.}} = 0$ b/w V & I

Page No.: / /
Date: / /

Purely Resistive Circuits (Lamp, bulb)

$\therefore \text{Inst. power} \Rightarrow P = VI$

$$= V_0 \sin \omega t \times I_0 \sin \omega t$$



$$= V_0 I_0 \sin^2 \omega t$$

$$= \frac{V_0 I_0}{2} [2 \sin^2 \omega t]$$

$$= \frac{V_0 I_0}{2} [1 - \cos 2\omega t]$$

$$= \frac{V_0 I_0}{2} - \frac{V_0 I_0}{2} \cos 2\omega t$$

Constant Part Pulsating Part

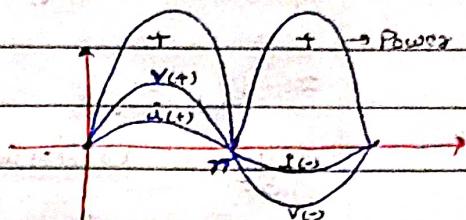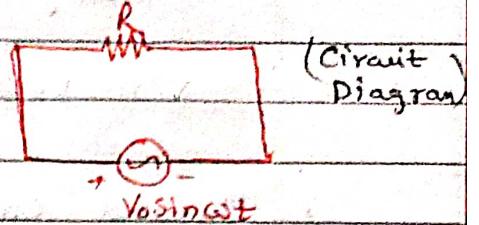

Wave diagram

+ Inst. power in Purely Resistive circuit is pulsating at double freqn -

So we take avg. Power -

$$P_{\text{avg}} = \frac{1}{\pi} \int_0^\pi P d\omega t = \frac{1}{\pi} \int_0^\pi \left[\frac{V_0 I_0}{2} - \frac{V_0 I_0}{2} \cos 2\omega t \right]$$

$$= \frac{1}{\pi} \frac{V_0 I_0}{2} [\omega +]_0^\pi$$

$$= \frac{V_0 I_0}{2}$$

$$= \frac{V_0}{\sqrt{2}} \frac{I_0}{\sqrt{2}}$$

$$P_{\text{avg}} = V_{\text{rms}} \cdot I_{\text{rms}}$$


Power factor \Rightarrow It is the Cosine of angle b/w V & I

for Pur. Resi. $\Rightarrow \cos \phi = \cos 0^\circ$

$$= 1$$

Purely Inductive Circuit

$$\bullet V = V_0 \sin \omega t$$

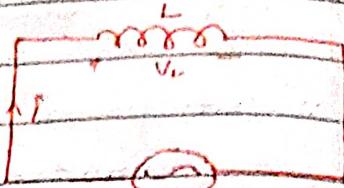


$$\Rightarrow \text{Induced emf} = L \frac{di}{dt} = V_L$$

$$\therefore V_L = V$$

$$L \frac{di}{dt} = V_0 \sin \omega t$$

$$\int di = \int \frac{V_0}{L} \sin \omega t dt + C$$

$V_0 \sin \omega t$

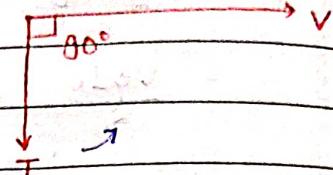

$\{ C \text{ is eventually zero so } \}$

$$i = \frac{V_0}{L} \left(-\frac{\cos \omega t}{\omega} \right)$$

$$= -\frac{V_0}{\omega L} \cos \omega t$$

$$i = \frac{V_0}{\omega L} \sin (\omega t - \pi/2)$$


$$i = i_0 \sin (\omega t - \pi/2)$$

\Rightarrow Current lags behind voltage by $\pi/2$ / 90° .

$$\Rightarrow (\phi)_{\text{Purely Ind.}} = 90^\circ$$

$$\therefore V_0 = i_0 \omega L$$
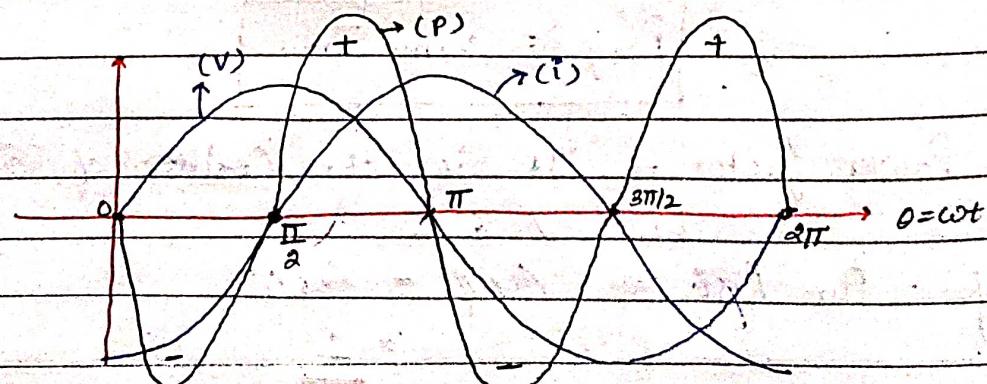
$$\Rightarrow \omega L = \frac{V_0}{i_0} = X_L$$



+ Power \Rightarrow Power Consumed by Inductor
- Power \Rightarrow Power Returned to Source

* In Pure Inductive Circuit net Power Consumed by
Inductor = 0.

Page No.:

(15)

Date: / /

Net Power \rightarrow

$$P = VI$$

$$\begin{aligned} &= V_0 \sin \omega t I_0 \sin (\omega t - \pi/2) \\ &= -V_0 I_0 \sin \omega t \sin (\pi/2 - \omega t) \\ &= -V_0 I_0 \sin \omega t \cos \omega t \\ &= -\frac{V_0 I_0}{2} \underbrace{\sin 2\omega t}_{\text{Pulsative in nature}} \end{aligned}$$

Pulsative in nature

$$P_{avg} = \frac{1}{T} \int_0^T P dt$$

$$= 0$$

$Z \rightarrow$ Impedance is like Complex so we use \angle for Z based on it.

Page No. _____

Date: / /

"Series R-L Circuit"


* In Series circuit -

Current is constant so

It is usually taken as reference.

$$\bar{V} = \text{Supply Voltage}$$

$$= \bar{V}_R + \bar{V}_L$$

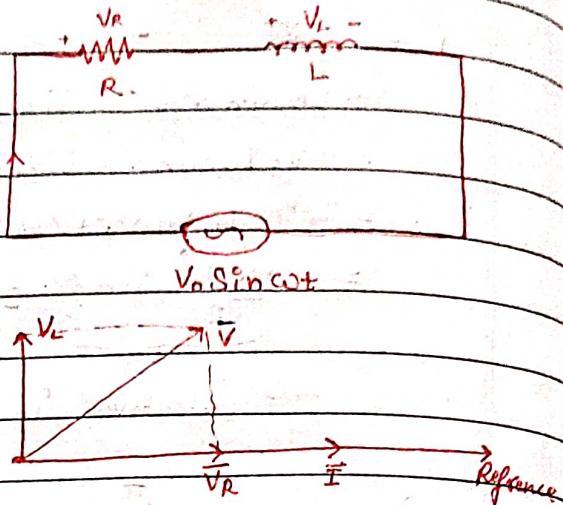

$$|\bar{V}|_{\text{magn.}} = \sqrt{\bar{V}_R^2 + \bar{V}_L^2}$$

$$\bar{I}\bar{Z} = \bar{I}R + \bar{I}(jX_L)$$

↳ Impedance

$$\bar{Z} = R + jX_L$$

$$|Z|_{\text{magn.}} = \sqrt{R^2 + X_L^2}$$

Voltage Triangle

$$\begin{aligned} \bar{I}\bar{Z} &= \bar{V} \\ V_L &= I X_L \\ V_R &= I R \end{aligned}$$

$$V_L = I X_L$$

$$\begin{aligned} \bar{I}\bar{Z} &= \bar{V} \\ V_L &= I X_L \\ V_R &= I R \end{aligned}$$

$$\begin{aligned} S &= I^2 Z \\ Q_L &= I^2 X_L \\ P &= I^2 R \end{aligned}$$

Impedance Triangle

$$\begin{aligned} \bar{Z} &= R + jX_L \\ |Z| &= \sqrt{R^2 + X_L^2} \end{aligned}$$

Power Factor

$$\cos \phi = R/Z$$

&

$$\cos \phi = P/S$$

Avg Power = $P = \text{Active Power} / \text{Real Pow.} / \text{True Power} = I^2 R$

$$P = I^2 R = V I \cos \phi$$

↳ Power Consumed in Resistive of the Circuit

Unit → watt, kw., mega watt

Q_L = Reactive Power = I²X_L = VI sin φ


↳ Power Consumed in Reactance of the Circuit

Unit = VAR, KVAR, MVAR

S = Apparent Power = I²Z = VI

↳ Power consumed by the Impedance (Z) of Circuit.

Unit = VA, KVA

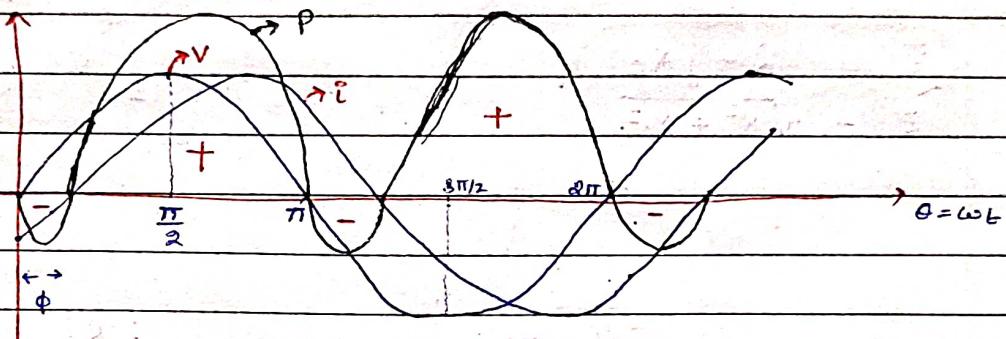

P+ >> P-

Instantaneous Power →

$$P = V \times I$$

$$= V_0 \sin \omega t \times I_0 \sin (\omega t - \phi)$$

$$= \frac{V_0 I_0}{2} [2 \sin \omega t \sin (\omega t - \phi)]$$

$$= \frac{V_0 I_0}{2} [\cos \phi - \cos (2\omega t - \phi)]$$

$$P = \underbrace{\frac{V_0 I_0}{2} \cos \phi}_{\text{Fixed Part}} - \underbrace{\frac{V_0 I_0}{2} \cos (2\omega t - \phi)}_{\text{Pulsating Part}}$$

Fixed Part Pulsating Part

Avg Power → P_{avg} = $\frac{1}{T} \int_0^T P dt$

$$= \frac{V_0 I_0}{2} \cos \phi = V_{rms} I_{rms} \cos \phi$$

$$\star R-L \Rightarrow Z = R+jX_L$$

$$\star R-C \Rightarrow Z = R-jX_C$$

Page No.:

Date: / /

"R-C Series Circuit"

(I leads V by ϕ)




$$\bar{V} = \bar{V}_R + \bar{V}_C$$

$$\text{Max } V = \sqrt{V_R^2 + V_C^2}$$

$$\bar{Z} = R - jX_C$$

$$Z = \sqrt{R^2 + X_C^2}$$

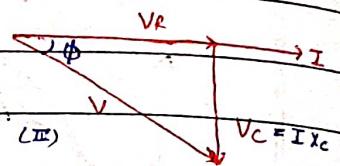
$$V_{\text{Instant}} = V \sin(\omega t)$$



$$\Rightarrow \bar{V}_R = IR$$

$$\bar{V}_C = IX_C$$

$$V = IZ$$

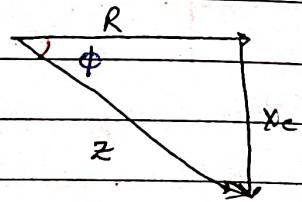

Impedance Triangle

$$P_{\text{avg}} = VI \cos \phi$$

$$(\text{True Power}) P = I^2 R = VI \cos \phi$$

$$Q_C = I^2 X_C = VI \sin \phi$$

$$(\text{Apparent Power}) S = I^2 Z$$

↳ Reactive Power (Capacitive)

(Power Triangle)

"Series R-L-C Circuit"

$+V_R$ $+V_L$ $+V_C$

R L C

\rightarrow V_{sinusoid}

\rightarrow V_L

\rightarrow V_R I Ref.


\rightarrow V_C

Phase Diagram

(Case 1: if $(X_L > X_C)$)

$$V_L > V_C$$

then it'll behave like R-L
Circuit

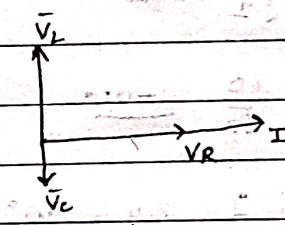


$\phi > 0$

(Case 2: if $(X_L < X_C)$)

$$V_L < V_C$$

then it'll behave like R-C
Circuit.

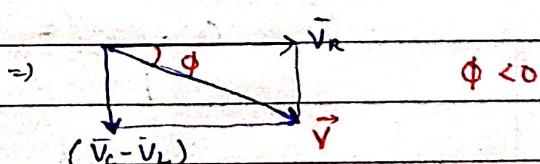

$\phi < 0$

Ques: The Voltage and Current through a circuit element are -


$$V = 100 \sin(314t + 45^\circ)$$

$$I = 10 \sin(314t + 315^\circ)$$

- i) Identify the Circuit element
- ii) Find the value of element
- iii) Find Power Consumed

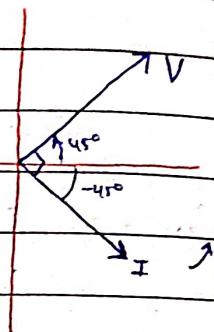i) $V = \frac{100}{\sqrt{2}} \angle 45^\circ$

$I = \frac{10}{\sqrt{2}} \angle -45^\circ$



$\therefore V$ lead I by 90°

\Rightarrow Pure Inductor Circuit

ii) $Z = \frac{V}{I} = \frac{100/\sqrt{2} \angle 45^\circ}{10/\sqrt{2} \angle -45^\circ}$

$$= 10 \angle 1490^\circ$$

$$jX_L = j(10)$$

$$X_L = 10$$

$$\omega L = 10$$

$$L = \frac{10}{314} = 0.03 \text{ Henry}$$

iii) $P_{avg} = 0$

$$P_{avg} = -V_0 I_0 \sin 2\omega t$$

$$= -500 \sin(628t)$$

While addn & Sub. use Rect. & by Mult. & Div. use

Polar form $\Rightarrow \frac{z_1}{z_2} = \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = | \frac{z_1}{z_2} | \angle \theta_1 - \theta_2$

Page No.:

Date: / /

21

Ques: Find Circuit element by given V & I

$$V(t) = 9 \sin t$$

$$I(t) = 3 \cos t$$

$$\Rightarrow \omega = 1 \text{ rad/sec}$$

$$i(t) = 3 \sin(\omega t + \pi/2)$$

$$= 3 \sin(t + \pi/2)$$

I leads V by $90^\circ \Rightarrow$ Pure Capac.

Phasor \rightarrow

$$\bar{V} = \frac{9}{\sqrt{2}} \angle 0^\circ$$

$$\bar{I} = \frac{3\sqrt{3}}{\sqrt{2}} \angle 90^\circ$$

$$Z = \frac{\bar{V}}{\bar{I}} = 3 \angle -90^\circ$$

$$= -j(3)$$

$$Z = jX_C = -j(3)$$

$$X_C = 3$$

$$\frac{1}{C} = 3$$

$$C = \frac{1}{3} \text{ Farad}$$

Ques: A 50Hz 230V is applied on 26.5 μF

Capacitor -

i) write time expressions of volt Current.

ii) Find Max energy stored in Capacitor

$$\Rightarrow \omega = 2\pi f = 100\pi$$

$$V_{max} = 230V$$

$$C = 26.5 \times 10^{-6} F$$

$$V = 230\sqrt{2} \sin(100\pi t)$$

$$X_C = \frac{1}{\omega C} = \frac{1}{100\pi \times 26.5 \times 10^{-6}}$$

$$= 120.1 \Omega$$

$$\bar{I} = \frac{\bar{V}}{Z}$$

$$= \frac{230 \angle 0^\circ}{120.1 \angle -90^\circ}$$

$$= 1.9148 \angle 90^\circ$$

$$I = 1.9148 \sqrt{2} \sin(100\pi t + \pi/2)$$

$$ii) \omega = \frac{1}{2} CV_0^2$$

$$= \frac{1}{2} \times 26.5 \times 10^{-6} (230\sqrt{2})^2$$

$$= 1.4 \text{ J}$$

Ques:

$$V = 200\sqrt{2} \cos 500t$$

$$P = 250 \text{ W}$$

$$PF = \cos \phi = 0.7 (\text{lag})$$

$$Q = ?$$

$$P = VI \cos \phi$$

$$I = P = \frac{250}{200 \times 0.7} = 1.7857 \text{ Amps}$$

$$\therefore Q = VI \sin \phi$$

$$= 200 \times 1.7857 \sqrt{1 - (0.7)^2}$$

$$= 255.03$$

Ques. If we apply 10 volt DC to RL circuit, we'll get 5 amp Current. Now if we apply 10V AC to the same RL circuit, we will get 3 amp Current. Find inductance of inductor. ($f = 50 \text{ Hz}$)

$$\therefore R = \frac{V}{I} \text{ for D.C.}$$

$$R = \frac{10}{5} = 2 \Omega$$

$$Z = \frac{V}{I} \text{ for AC}$$

$$\sqrt{R^2 + X_L^2} = \frac{10}{3}$$

$$X_L^2 = \frac{100}{9} - R^2 = \frac{100}{9} - 4$$


$$X_L = \sqrt{\frac{64}{9}} = \frac{8}{3}$$

$$\omega L = \frac{8}{3}$$

$$L = \frac{8}{3} \times \frac{1}{2\pi f} = \frac{8}{3 \times 100\pi} = 8.4 \text{ m Henry}$$

(Voltage Resonance)

Series Resonance

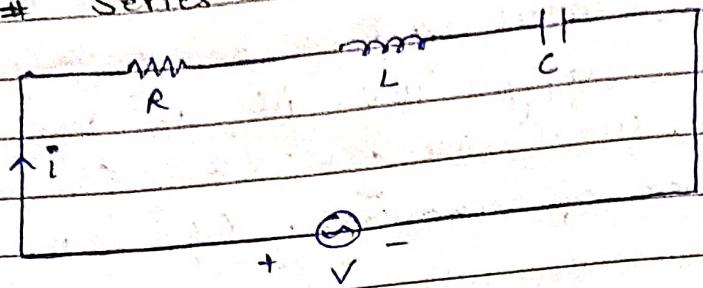

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z_{\min} = R$$

Conditions for Resonance

→ for some freqn $X_L = X_C$;

i) Net Reactance $X = X_L - X_C = 0$


ii) Impedance $Z = R$

iii) $I_{\max} = V/R$

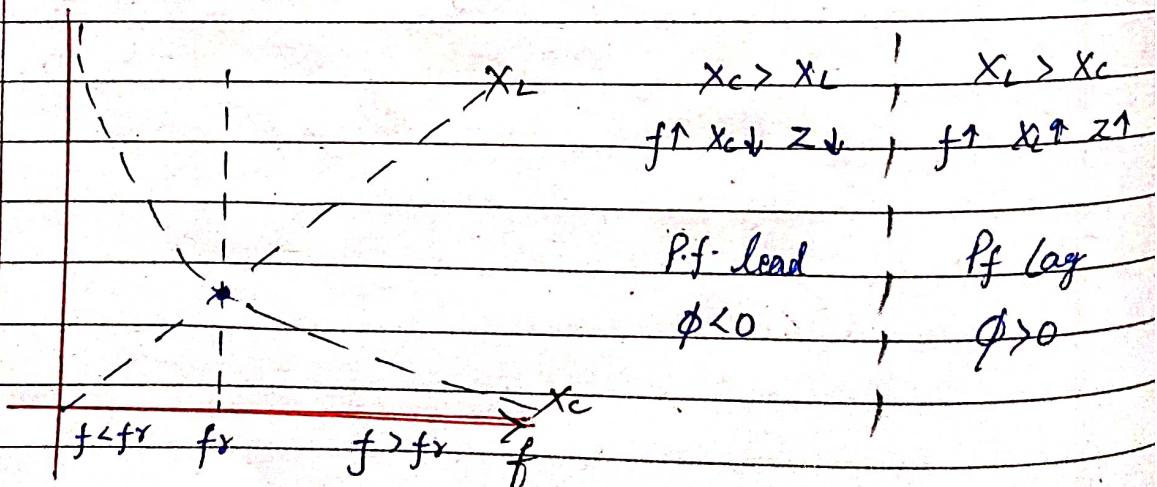iv) $\cos \phi = 1$

f_r = Resonant freqn = freqn at which Resonance occurs.



$$X_L = X_C \Rightarrow f_r = \frac{1}{2\pi\sqrt{LC}} ; \omega_r = \frac{1}{\sqrt{LC}}$$



* P.F. if $I > V$ then ~~leads~~ (leads)
if $I < V$ then ~~lags~~ (lags)

o Cutoff freqn \rightarrow point at which $i \rightarrow \frac{i_0}{\sqrt{2}}$

Page No.: 25
Date: / /

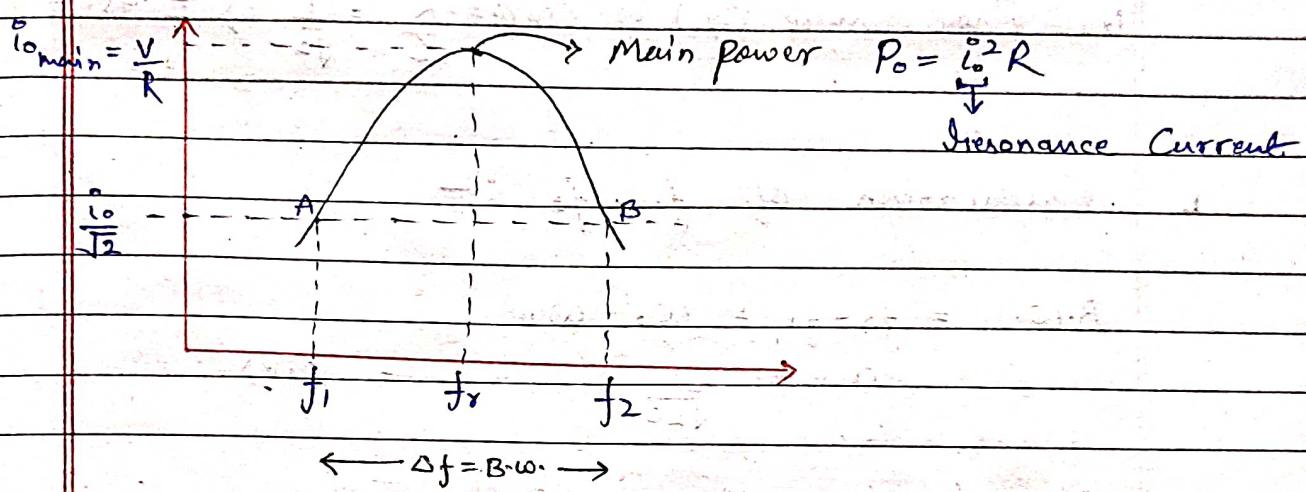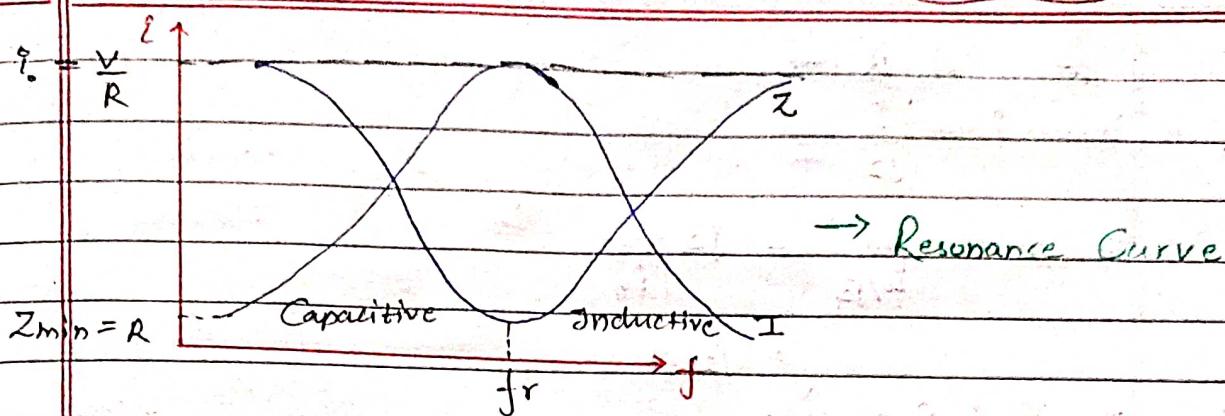

■ Band width = Band of frequencies which lies btw 2 points on either sides of resonant frequency (f_r) .

$$\Delta f = f_2 - f_1 ;$$

$$f_2 = f_r + \frac{\Delta f}{2}$$

* $f_1 = \text{lower Cutoff freqn}$

or

$$f_1 = f_r - \frac{\Delta f}{2}$$

Lower half power freqn

at f_1, f_2 (half power points)

$$i = i_0 / \sqrt{2}$$

at A, B

* $f_2 = \text{Upper Cutoff freqn}$

$$P = \frac{1}{2} i_0^2 R$$

$$= \frac{P_0}{2}$$

at A, B \rightarrow

$$i) i = \frac{i_0}{\sqrt{2}}$$

$$ii) Z = \frac{V_0}{i_0/\sqrt{2}} = \sqrt{2} \frac{V_0}{i_0}$$

$$= \sqrt{2} R$$

$$iii) P_A = P_B = P_0/2$$

$$iv) \text{Phase angle } (\phi) \Rightarrow \cos \phi = \frac{R}{Z} = \frac{1}{\sqrt{2}} \Rightarrow +45^\circ = \phi$$

lead
lag

□ Calculation of f_1, f_2 :-

$$\text{B.W.} = f_2 - f_1 = \omega_2 - \omega_1$$

$$\omega_r = \frac{1}{\sqrt{LC}} \quad \text{(iv)}$$

$$\text{at } f_1, f_2 \rightarrow i = i_0/\sqrt{2}$$

$$\frac{i_0}{\sqrt{2}} = \frac{V}{Z} \rightarrow \frac{i_0}{\sqrt{2}} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \quad \left\{ \because i_0 = \frac{V}{R} \right.$$

$$\sqrt{2} R = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L - X_C = \pm R \quad \text{--- (i)}$$

* At Half Power Points net reactance of the circuit is equal to resistance of circuit

$$\omega_2 L - \frac{1}{\omega_2 C} = -R \quad \text{--- (ii)}$$

$$\omega_2 L - \frac{1}{\omega_2 C} = R \quad \text{--- (iii)}$$

eqn (ii) + (iii)

$$\omega_1 L - \frac{1}{\omega_1 C} + \omega_2 L - \frac{1}{\omega_2 C} = 0$$

$$L(\omega_1 + \omega_2) - \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} \right) \frac{1}{C} = 0$$

$$(\omega_1 + \omega_2) L - \frac{(\omega_1 + \omega_2)}{\omega_1 \omega_2 C} = 0$$

$$1 - \frac{1}{\omega_1 \omega_2 L C} = 0$$

$$\omega_1 \omega_2 = \frac{1}{LC} \quad \text{--- (v)}$$

Comparing (4) & (5) \rightarrow

$$\omega_s^2 = \omega_1 \omega_2$$

$$f_s^2 = f_1 f_2$$

Subtracting (ii) - (iii) \rightarrow

$$\left(\omega_2 L - \frac{1}{\omega_2 C} \right) - \left(\omega_1 L - \frac{1}{\omega_1 C} \right) = R - (-R)$$

$$L(\omega_2 - \omega_1) + \left(\frac{1}{\omega_1} - \frac{1}{\omega_2} \right) \frac{1}{C} = 2R$$

$$(\omega_2 - \omega_1) \left[1 + \frac{1}{\omega_1 \omega_2 L C} \right] = \frac{2R}{L}$$


$$(\omega_2 - \omega_1) \left[1 + \frac{LC}{LC} \right] = \frac{2R}{L} \quad \left. \begin{array}{l} \\ \end{array} \right\} \because \omega_1 \omega_2 = \frac{1}{LC}$$

* $\Delta \omega = \frac{R}{L} \Rightarrow \text{Bandwidth}$

* $\Delta f = \frac{R}{2\pi L}$

$$\Rightarrow \omega_1 = \omega_r - \frac{\Delta\omega}{2} \quad \text{--- (1)}$$
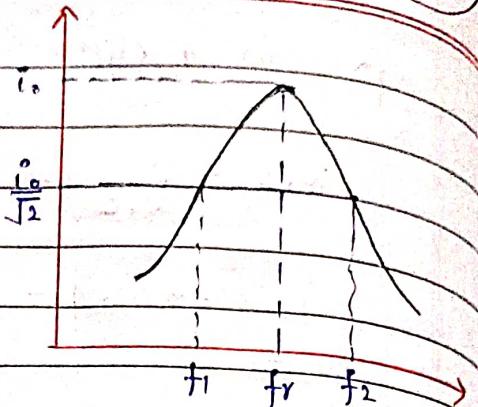
$$\Rightarrow \omega_2 = \omega_r + \frac{\Delta\omega}{2} \quad \text{--- (2)}$$



$$\omega_1 = \omega_r - \frac{R}{2L}$$

$\leftarrow \Delta f \rightarrow$

$$\omega_2 = \omega_r + \frac{R}{2L}$$

$$f_1 = f_r - \frac{R}{2L(2\pi)}$$

$$f_2 = f_r + \frac{R}{2L(2\pi)}$$

"At Resonance" \Rightarrow

Quality factor (Q_x) \Rightarrow Voltage Magnification factor.

$Q_x \uparrow$

$\Rightarrow V_L \uparrow V_C \uparrow$

it is ratio of V_L or V_C to Source Voltage.

$$Q_x = \frac{V_L}{V}$$

$$Q_x = \frac{V_C}{V}$$

$$= \frac{IX_L}{IR}$$

$$= \frac{IX_C}{IR}$$

*
$$Q_x = \frac{\omega_r L}{R}$$

*
$$Q_x = \frac{1}{\omega_r C R}$$

$$\Rightarrow \frac{R}{L} = \frac{\omega_r}{Q_x}$$

$$\Rightarrow Q_x = \frac{\omega_r}{\Delta\omega}$$

Similarly

$$Q_x = \frac{f_r}{\Delta f}$$


$$\therefore Q_x = \omega_0 \frac{L}{R}$$

$$= \frac{1}{\sqrt{LC}} \times \frac{L}{R}$$

$$Q_x = \frac{1}{R} \sqrt{\frac{L}{C}}$$

* Significance of Q.f. \rightarrow it is measure of sharpness or selectivity

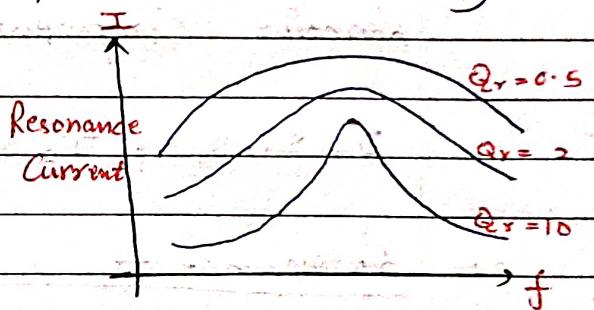\therefore Selectivity: It is the ability of RLC circuit to select any particular signal from group of signals.



Series RLC Circuit \rightarrow Radio receiver as accepter circuit

In series \Rightarrow


* $Z = R + j(X_L - X_C)$

* & at Reso \rightarrow

$\text{Imag}[Z] = 0$

" Parallel Resonance (Anti Reso. or Current Res.)

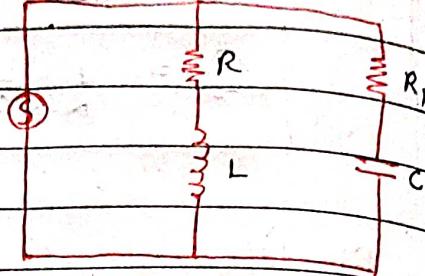when Resistive Component of Circuit becomes zero this circuit is said to be in Resonance.




Reactive Component of Current \rightarrow

$$I_1 \sin\theta_1, I_2 \sin\theta_2$$


at Resonance \rightarrow

$$I_1 \sin\theta_1 = I_2 \sin\theta_2$$

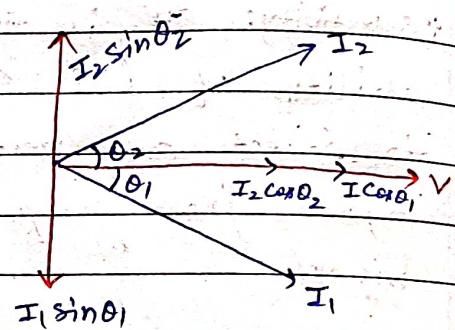

$$Z_1 = R + jX_L$$

$$Z_2 = R - jX_C$$

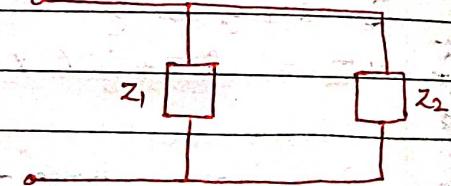


□ Calculation of Resonant freqn \rightarrow

$$\text{Admittance} \rightarrow (Y) = \frac{1}{Z}$$

$$Y = Y_1 + Y_2$$
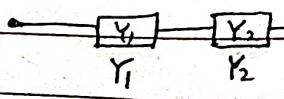
$$Y = \frac{1}{R+jX_L} + \frac{1}{R-jX_C}$$



$$Y = \frac{R-jX_L}{R^2+X_L^2} + \frac{R+jX_C}{R^2+X_C^2} \quad \text{--- (1)}$$

$$\therefore Z = R + j(X_L - X_C)$$

$$\Rightarrow Y = \underline{G} + j \underline{B}$$

Conductance Susceptance

at Reso. in eqn ① \rightarrow

$$\text{Im}[Y] = 0$$

$$B_C = B_L$$

$$\frac{X_C}{R_1^2 + X_C^2} = \frac{X_L}{R^2 + X_L^2}$$

$$\frac{1}{\omega C \left(R_1^2 + \frac{1}{\omega^2 C^2} \right)} = \frac{\omega L}{R^2 + \omega^2 L^2}$$



$$\frac{\omega C}{\omega^2 C^2 R_1^2 + 1} = \frac{\omega L}{R^2 + \omega^2 L^2}$$

$$R^2 C + \omega^2 L^2 C = \omega^2 R_1^2 C^2 L + L$$

$$\omega^2 = \frac{1}{LC} \left[\frac{R^2 C - L}{R_1^2 C - L} \right]$$

$$\omega_s = \frac{1}{\sqrt{LC}} \sqrt{\frac{R^2 - L/C}{R_1^2 - L/C}}$$

□ Tank Circuit :-

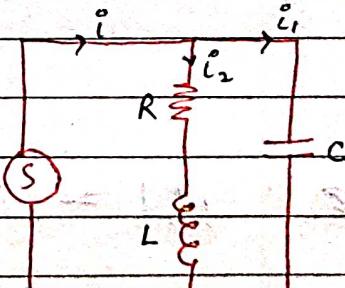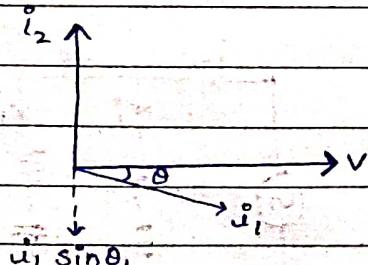

$$f_r = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R^2 - 4C}{R_1^2 - L/C}}$$

at Reso \rightarrow

$$i_2 = i_1 \sin \theta_1$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \frac{R^2}{L^2}$$

$$\frac{V}{Z} \times \frac{X_L}{Z} = \frac{V}{X_C}$$

$$\Rightarrow Z^2 = X_L X_C$$

$$Z = \sqrt{L/C}$$

$$i = i_1 \cos \theta + i_2 \sin \theta$$

$$i = \frac{V}{Z} \times \frac{R}{Z}$$

$$i = VR/2Z$$

$$\frac{Z^2}{R} = \frac{L}{RC}$$

$$\therefore \frac{V}{i} = Z_0$$

$$Z_0 = \frac{L}{RC}$$

dynamic impedance

imp. Points (parallel Imp.)

① Net Susceptance = 0

$$(B = 0)$$

$$(Z_0 = \frac{L}{RC})$$

② Admittance = Conductance

$$P_f = 1$$


③ Pure Resistive

$$(C_{min} = \frac{V}{Z_0})$$

④ $Y_{min} \rightarrow Z_{max} \rightarrow I_{max}$

$$(V/(4RC))$$

⑤ $|i_s| \approx |i_2| > i_{supply}$

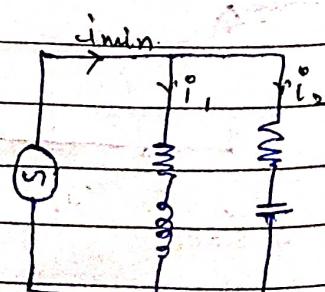

Current through capacitor and inductor is greater as compared to supply current that's why Current Resonance.

② Also called Resistor circuit because at Resonance line current and i_B minimum and Rejected

Current Magnification factor -

$$Q_r = \frac{i_L}{i}$$

$$Q_r = \frac{i_o}{i}$$

$$\left\{ \begin{array}{l} i_L = i_1 \\ i_o = i_2 \end{array} \right\}$$

$$Q_r = \frac{L}{R} \sqrt{\frac{L}{C}} \quad (Q_r = \frac{V_L}{V} = \frac{V_C}{V})$$