
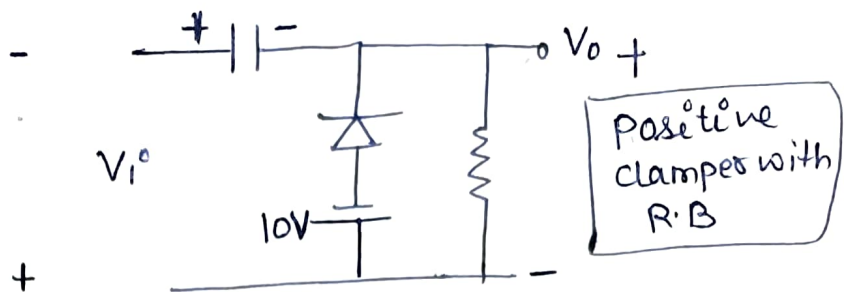


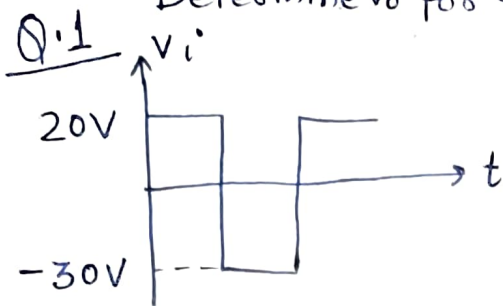Determine  $V_o$  for the n/w of fig. for the input indicated.



In -ve half cycle the diode is F.B, so it will be replace by a short circuit.

$$-V_i - V_c + 10 = 0$$


$$-30 - V_c + 10 = 0$$

$$-20 - V_c = 0$$

$$-V_c = 20$$


$$V_c = -20$$

$$V_o = -10$$

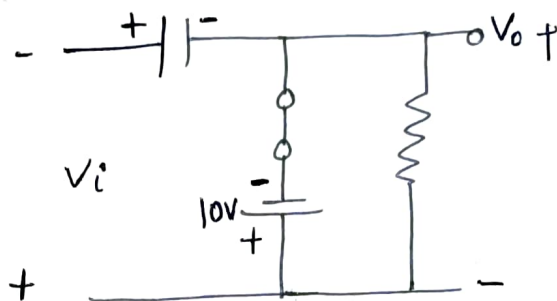

In +ve half cycle the diode will be R.B, so it will replace by o.c, and then

Apply KVL

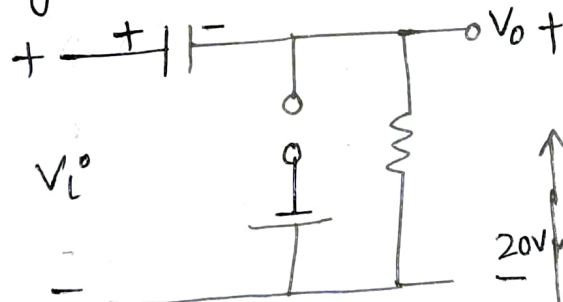

$$V_i - V_c - V_o = 0$$


$$30 + 20 - V_o = 0$$


$$40 - V_o = 0$$

$$40 - V_o = 0$$

$$+V_o = 40$$

$$V_o = 40$$

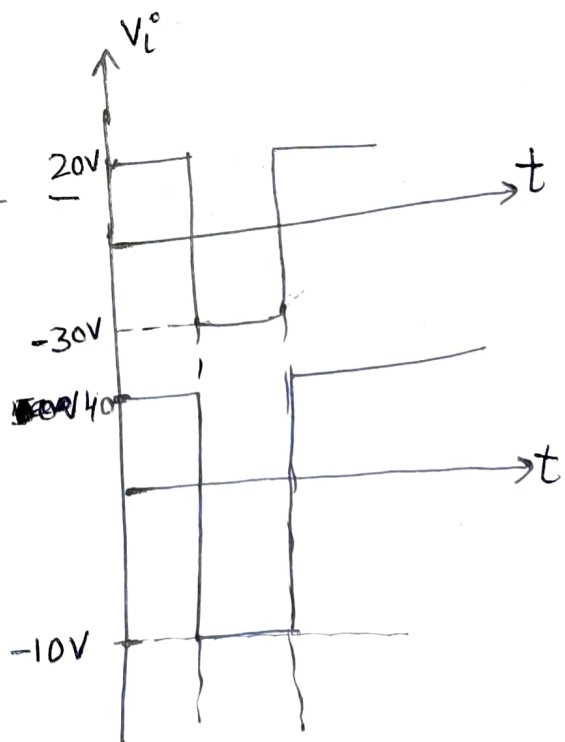

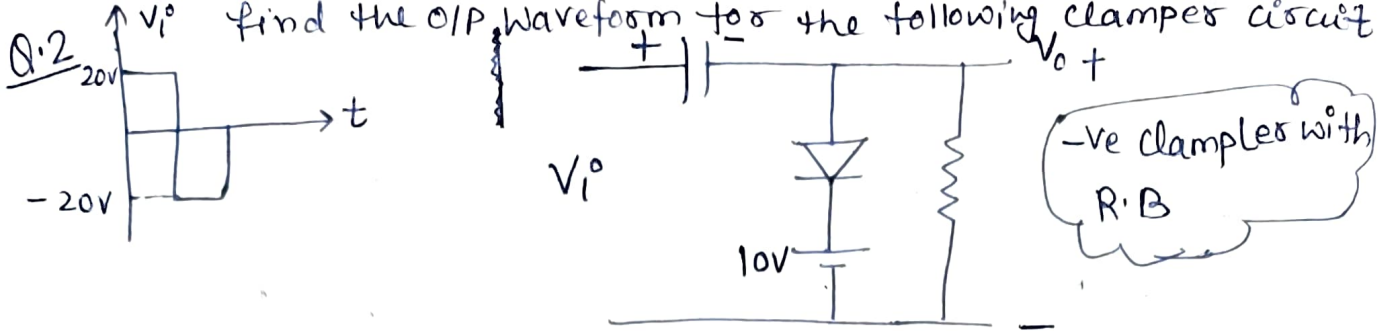

In +ve half cycle the diode will be F.B, so it will be replace by short circuit and then Apply KVL.


$$V_i - V_C - 10 = 0$$

$$20 - V_C - 10 = 0$$


$$10 - V_C = 0$$

$$-V_C = -10$$

$$V_C = 10, V_o = 10$$

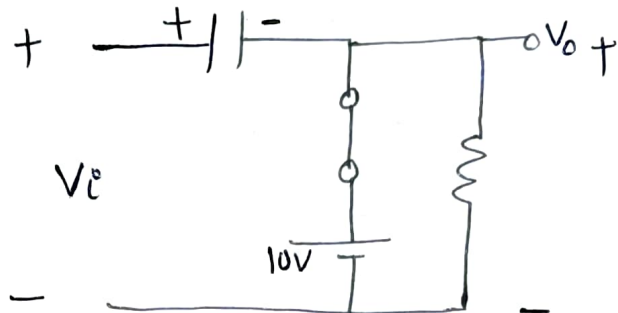

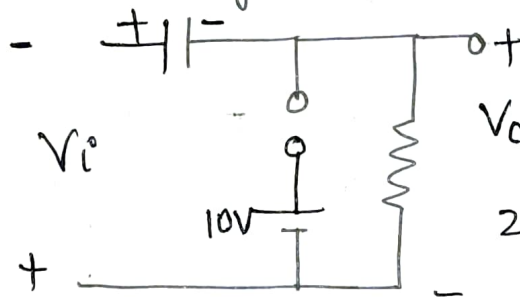In -ve half cycle the diode will be R.B, so it will replace by o.c, and then Apply KVL




$$-V_i - V_C - V_o = 0$$

$$-20 - 10 - V_o = 0$$



$$-30 - V_o = 0$$

$$-V_o = 30$$

$$V_o = -30$$

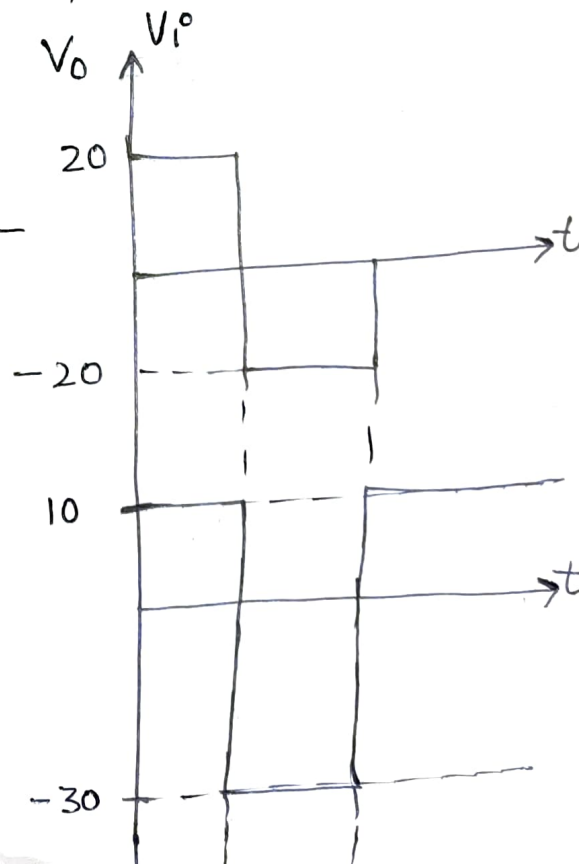


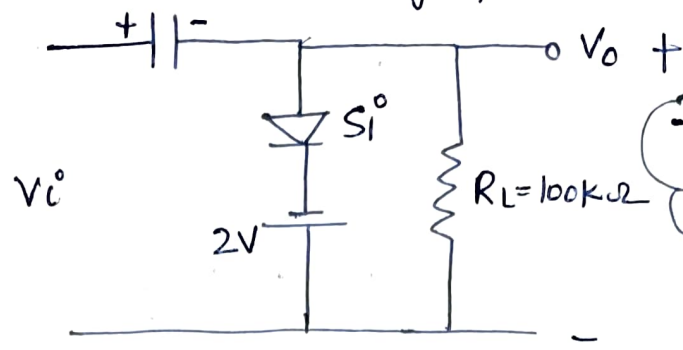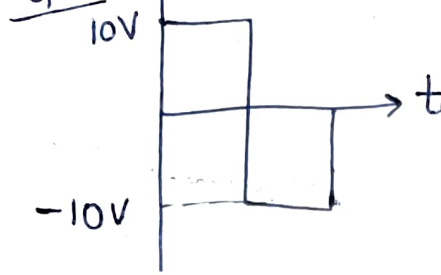Q.3 Determine  $V_o$  for the n/w of fig for the GIP indicated



-ve clamper with F.B

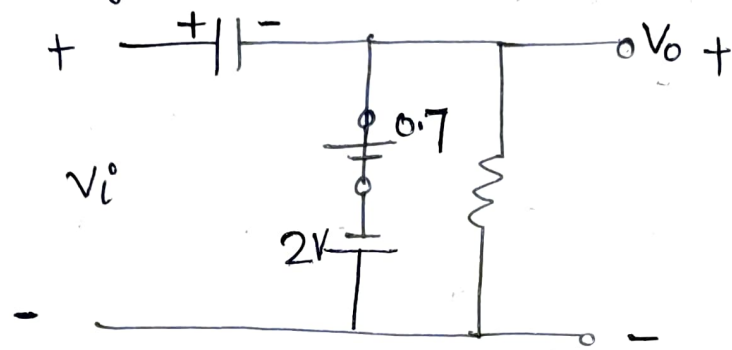In +ve half cycle the diode is F.B, so it will replace by S.C



~~$V_i - V_c - 0.7 = 0$~~   $V_i - V_c - 0.7 + 2 = 0$

~~$10 - V_c - 0.7 = 0$~~   $V_i - V_c + 1.3 = 0$

~~$10 - V_c = 0$~~   $10 - V_c + 1.3 = 0$


~~$V_c = 10$~~   $11.3 - V_c = 0$

~~$V_c = 11.3$~~   $-V_c = -11.3$

$V_c = 11.3V$

$V_o = -1.3V$

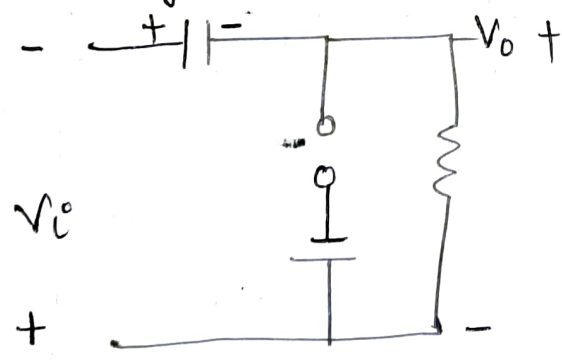In -ve half cycle the diode is R.B, so it acts as O.C



$-V_i - V_c - V_o = 0$

$-10 - 11.3 - V_o = 0$


$-21.3 - V_o = 0$

$V_o = -21.3V$



$-1.3 - (-21.3)$

$-1.3 + 20.3$

$20$

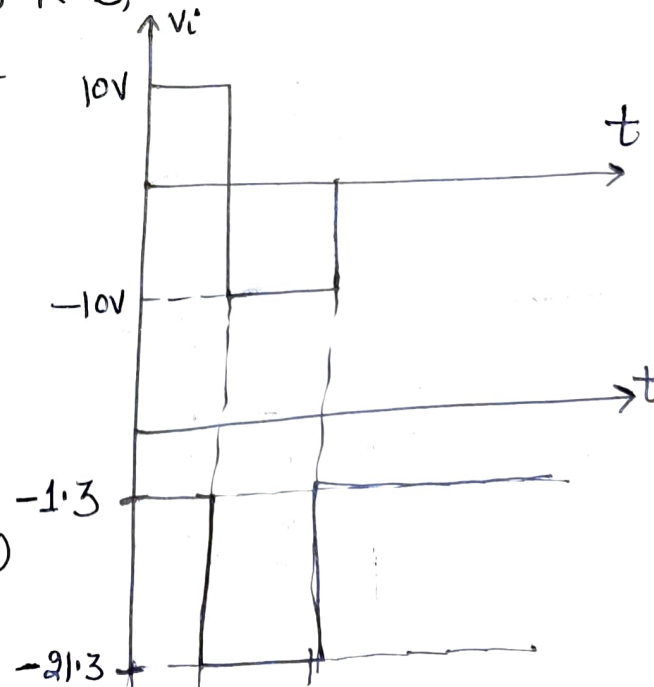


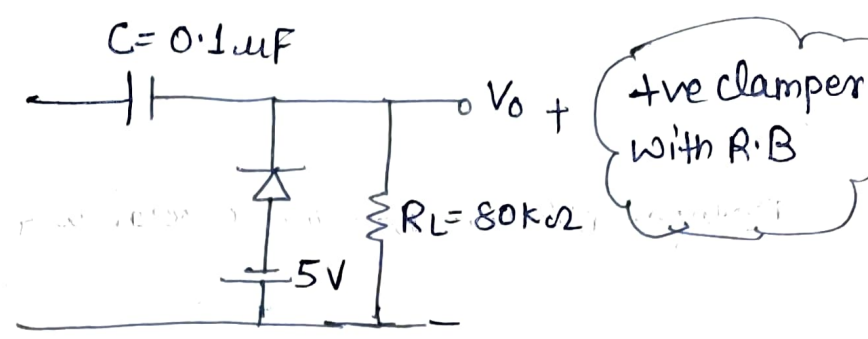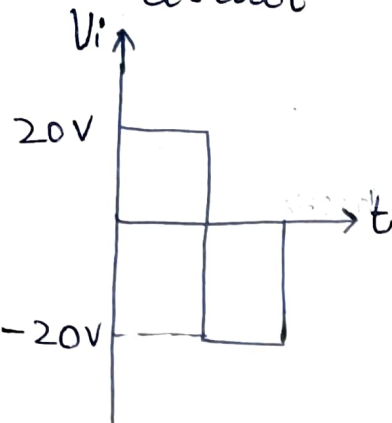Q.4 find the O/P waveform for the following clamper circuit.



In -ve half cycle the diode will be F.B, and act as a open ckt S.C.

Apply KVL

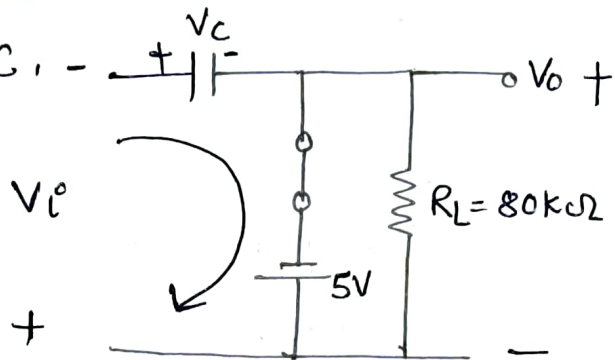

$$-V_i - V_c + 5 = 0$$


$$-20 - V_c + 5 = 0$$

$$-15 - V_c = 0$$

$$-V_c = 15$$

$$V_c = -15V, V_o = -5V$$

In +ve half cycle, D → R.B → O.C

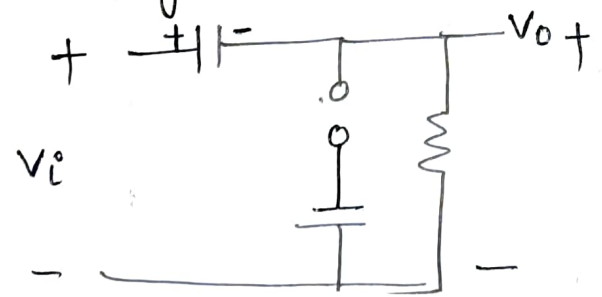



$$V_i - V_c - V_o = 0$$

$$20 - (-15) - V_o = 0$$

$$20 + 15 - V_o = 0$$



$$V_o = 35$$

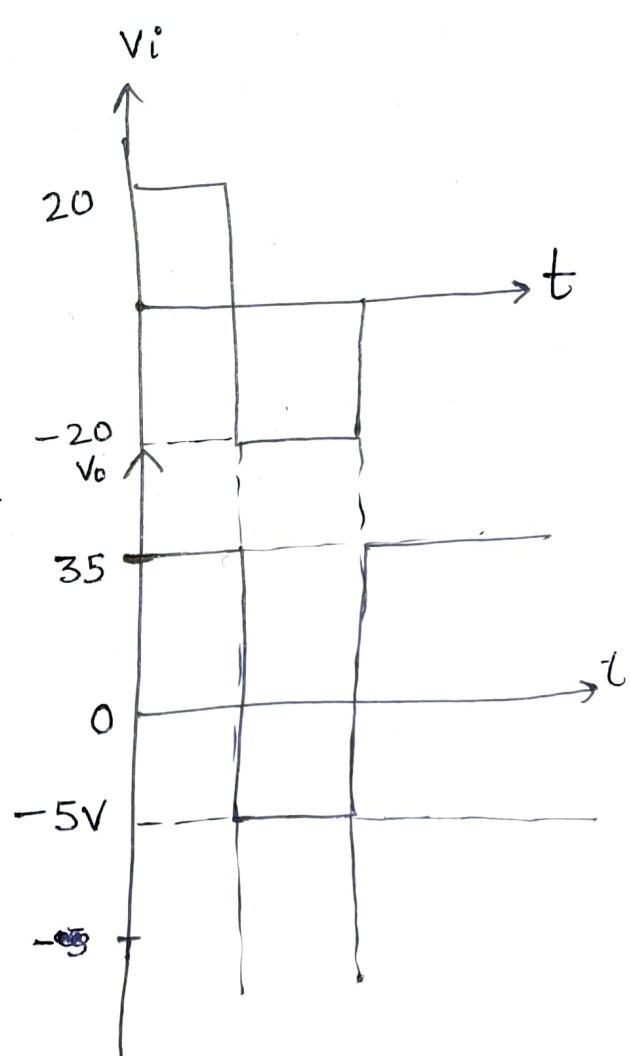

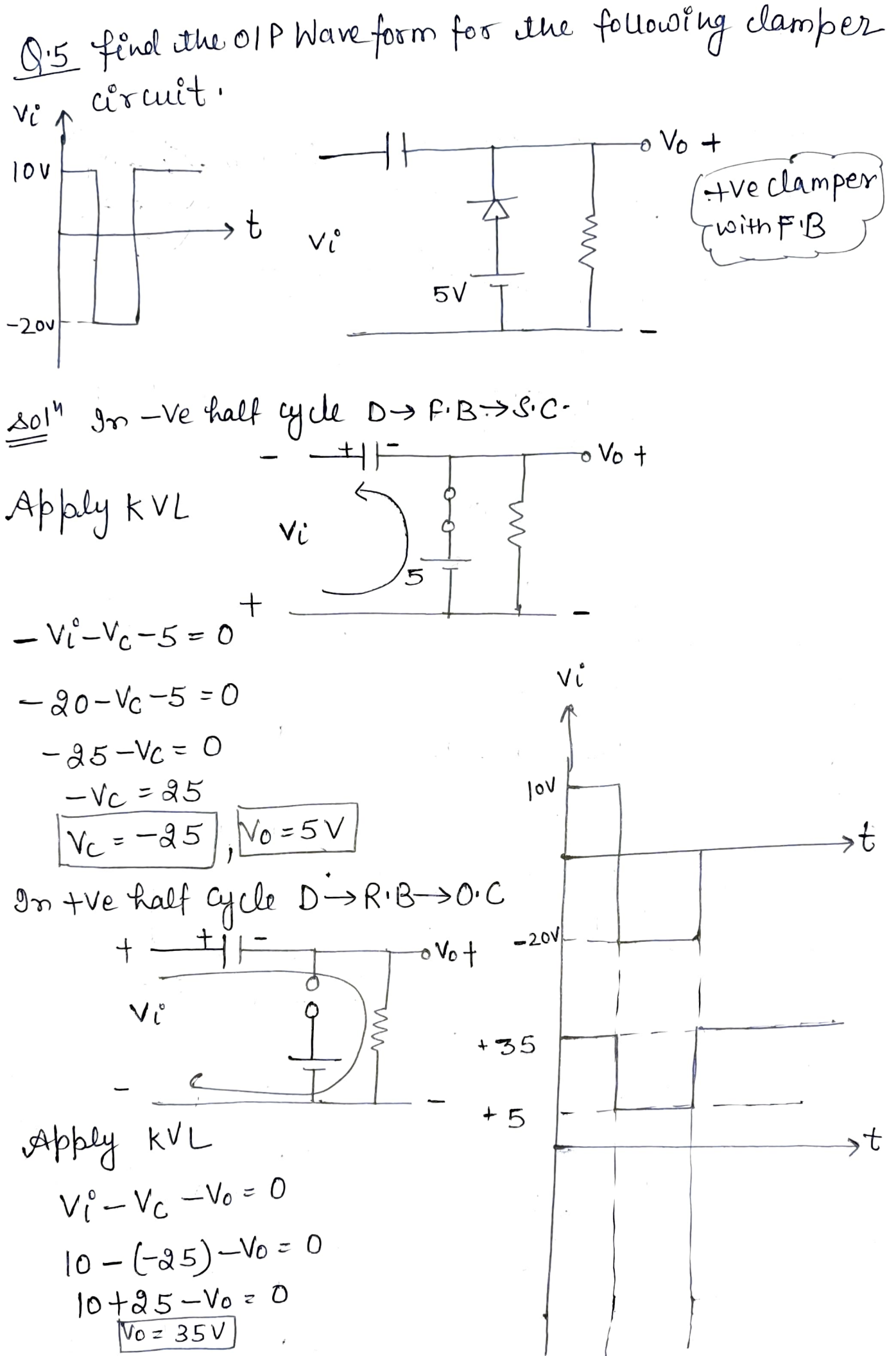




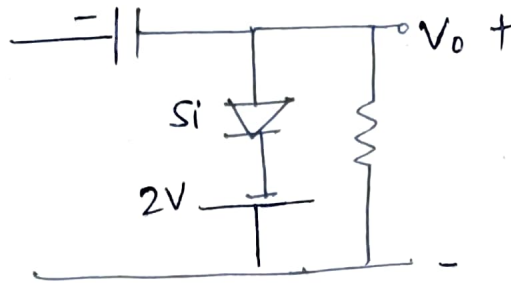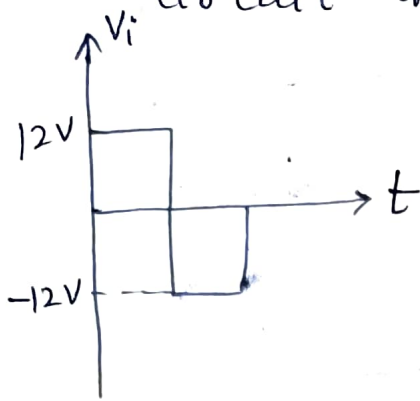Q.6 Determine the  $V_o$  for the following clamper circuit and sketch the o/p waveform.



-ve clamper with F.B

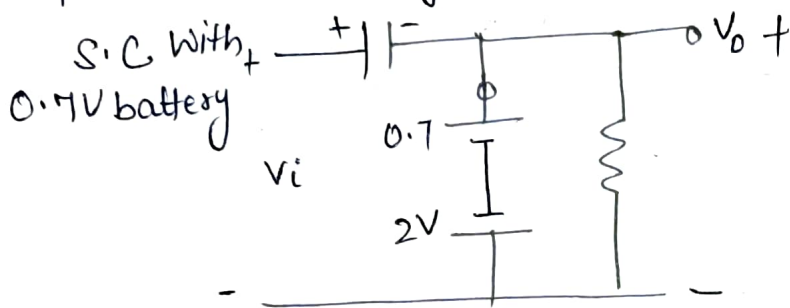For the +ve half cycle the diode will be F.B and replace by the




$$V_i - V_c - 0.7 + 2 = 0$$

$$12 - V_c - 1.3 = 0$$

$$V_c = 13.3V, V_o = -1.3V$$

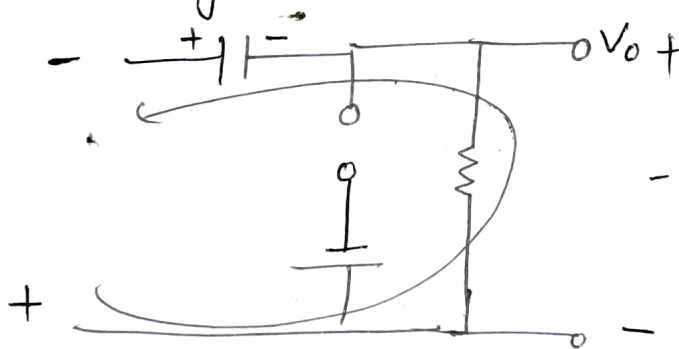For the -ve half cycle  $D \rightarrow R.B \rightarrow O.C.$



Apply KVL

$$-V_i - V_c - V_o = 0$$

$$-12 - 13.3 - V_o = 0$$

$$-25.3 - V_o = 0$$


$$-V_o = 25.3$$

$$V_o = -25.3$$



$$-1.3 - (-25.3)$$

$$-1.3 + 25.3$$

$$24V$$

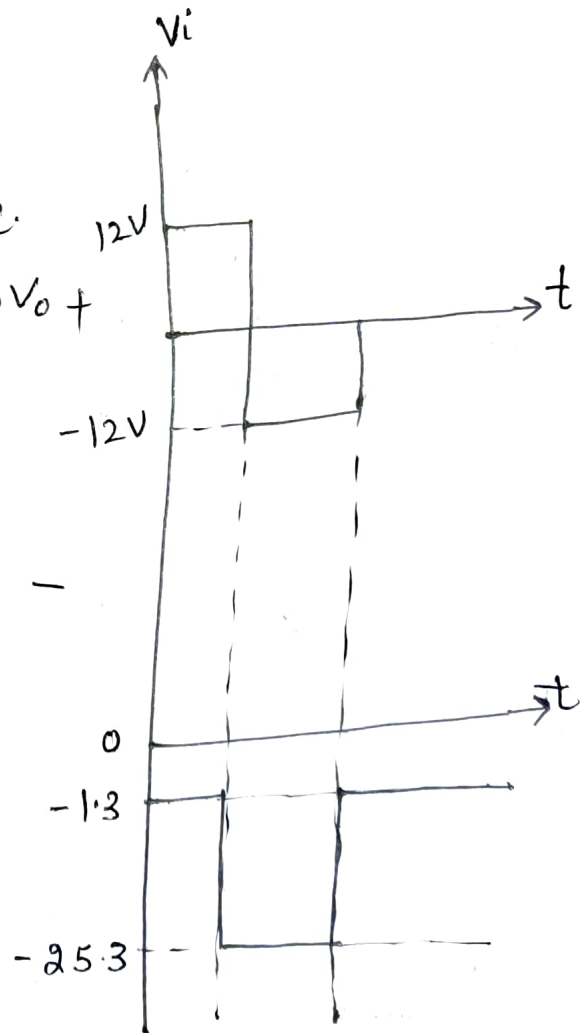


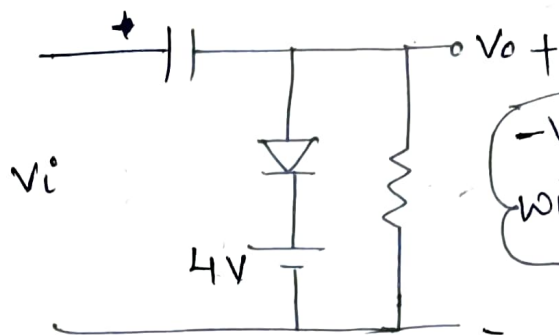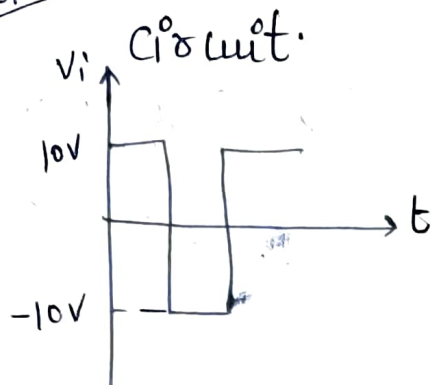Q.7 sketch the output waveform for the following clamper circuit.



-ve clamper  
with R.B

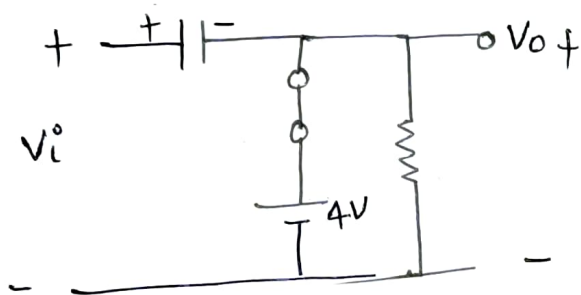For the +ve half cycle the Diode  $\rightarrow$  F.B  $\rightarrow$  S.C



$$V_i - V_C - 4 = 0$$

$$10 - V_C - 4 = 0$$


$$6 - V_C = 0$$

$$-V_C = -6$$

$$V_C = 6V$$

$$V_o = 4V$$

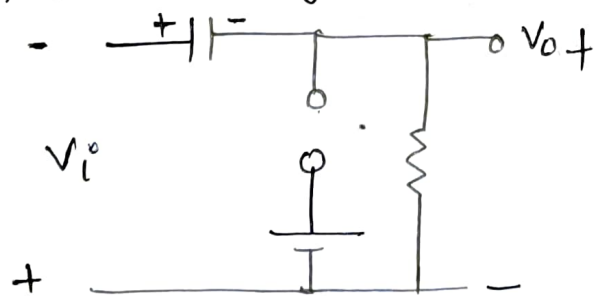For the -ve half cycle the Diode  $\rightarrow$  R.B  $\rightarrow$  O.C




$$-V_i - V_C - V_o = 0$$



$$-10 - 6 - V_o = 0$$

$$-16 - V_o = 0$$

$$V_o = -16V$$

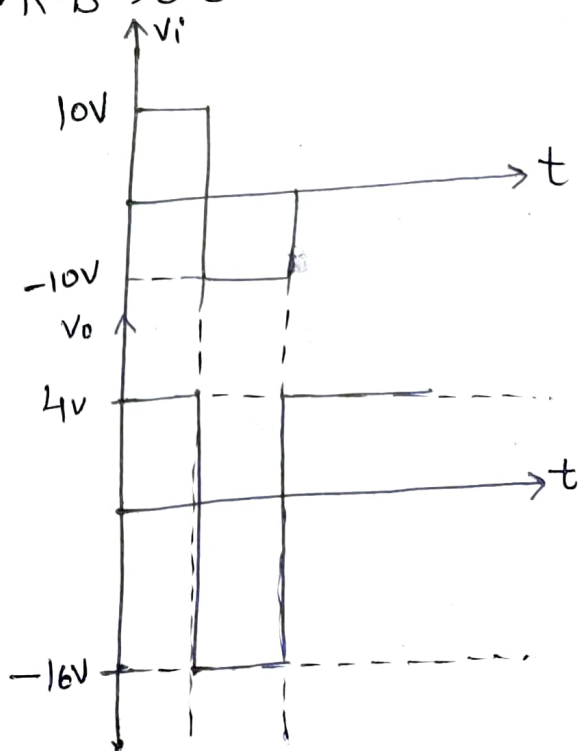


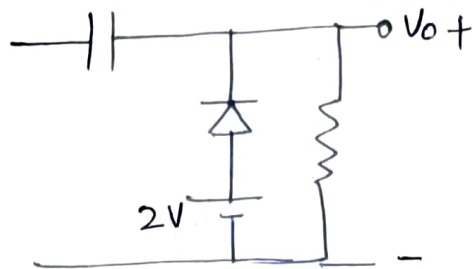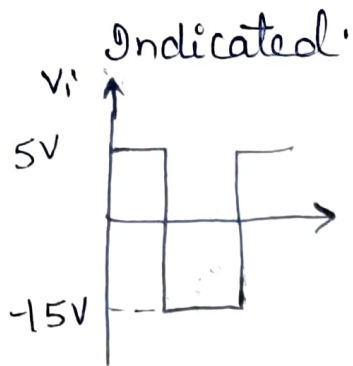Q.8 Determine  $V_o$  for the n/w of figure for one I/P



+ve clamper with  
F.B

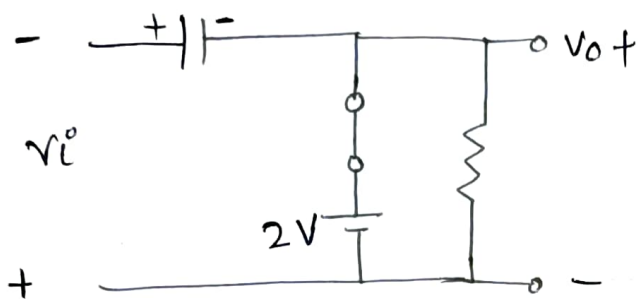for the -ve half cycle the Diode  $\rightarrow$  F.B  $\rightarrow$  S.C



$$-V_i - V_c - 2 = 0$$

$$-15 - V_c - 2 = 0$$



$$-17 - V_c = 0$$

$$-V_c = 17$$

$$V_c = -17$$

$$V_o = 2V$$

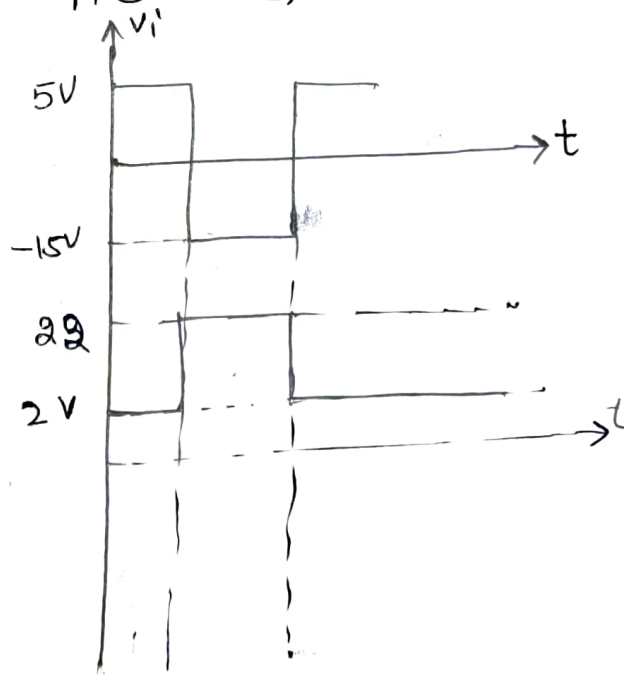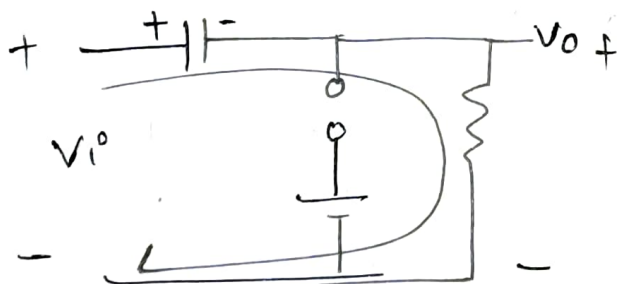for the +ve half cycle the diode is R.B  $\rightarrow$  O.C,



$$V_i - V_c - V_o = 0$$

$$5 - (-17) - V_o = 0$$

$$5 + 17 - V_o = 0$$

$$22 - V_o = 0$$

$$V_o = 22$$

$$V_o = 22$$